

In **quantum computing**, we can perform **simple addition using qubits** with **basic quantum gates**, usually with a **quantum ripple-carry adder** approach. For a beginner-friendly example, let's create a circuit to **add two 1-bit numbers**.

Simple 1-Bit Addition Using Quantum Gates

Goal: Add two numbers a and b (each 0 or 1) and get:

- Sum (s)
- Carry (c)

Truth table for 1-bit addition:

a b Sum (s) Carry (c)

0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Step 1: Quantum Circuit Setup

We need **3 qubits**:

1. $a \rightarrow$ first number
2. $b \rightarrow$ second number
3. carry/sum \rightarrow output

And **2 classical bits** to read the outputs.

Step 2: Gates for 1-Bit Adder

1. **CNOT gate** \rightarrow calculates **sum modulo 2 (XOR)**
 - $\text{sum} = a \text{ XOR } b$
2. **CCNOT (Toffoli) gate** \rightarrow calculates **carry**
 - $\text{carry} = a \text{ AND } b$

3. Quantum Circuit: Step-by-Step Explanation

4. 1. Qubits and Classical Bits

```
qc = QuantumCircuit(3,2)
```

3 qubits:

1. $q_0 \rightarrow$ represents input **a**
2. $q_1 \rightarrow$ represents input **b**
3. $q_2 \rightarrow$ represents **sum/carry output**

□ **2 classical bits:**

1. $c_0 \rightarrow$ stores **sum**
2. $c_1 \rightarrow$ stores **carry**

```
qc.x(0) # a=1
```

```
qc.x(1) # b=1
```

X gate flips a qubit from $|0\rangle \rightarrow |1\rangle$.

Here, we set $a=1$ and $b=1$ for this example.

If inputs were 0, we would not apply X.

Compute Sum (XOR)

```
qc.cx(0,2)
```

- `qc.cx(1,2)`

CNOT (controlled-NOT) gate: flips the target qubit if the control qubit is 1.

- **Step explanation:**

1. First CNOT(0,2) \rightarrow sum qubit flips if $a=1$
2. Second CNOT(1,2) \rightarrow sum qubit flips again if $b=1$

- **Result:** $\text{sum} = a \text{ XOR } b$

Example:

- $a=1, b=1 \rightarrow$ sum qubit flips twice \rightarrow ends up as 0 \rightarrow correct sum bit.

Compute Carry (AND)

- `qc.ccx(0,1,2)`
- **CCX (Toffoli gate):** controlled-controlled-NOT
- Flips the target qubit **only if both control qubits are 1.**
- **Purpose:** compute carry = $a \text{ AND } b$

Example:

- $a=1, b=1 \rightarrow$ both controls are 1 \rightarrow sum/carry qubit flips \rightarrow represents carry bit.

Measurement

`qc.measure(2,0) # sum`

`qc.measure(1,1) # carry`

Measures qubits into classical bits.

$q_2 \rightarrow c_0 \rightarrow$ sum

$q_1 \rightarrow c_1 \rightarrow$ carry

Now the outputs can be read as classical binary numbers.

Draw the Circuit

`qc.draw('text')`

1-Bit Quantum Subtractor Logic

Inputs: a (minuend), b (subtrahend)

Outputs:

- difference = $a \text{ XOR } b$
- borrow = $\text{NOT } a \text{ AND } b$

Truth Table:

a b Difference Borrow

0 0 0 0

0 1 1 1

1 0 1 0

1 1 0 0

Quantum Circuit Steps in Quirk**Step 1: Qubits**

- Use **3 qubits**:
 - $q_0 \rightarrow$ a (minuend)
 - $q_1 \rightarrow$ b (subtrahend)
 - $q_2 \rightarrow$ difference/borrow output

Step 2: Difference Calculation (XOR)

- Same as adder:

difference = $a \text{ XOR } b$

In Quirk:

1. CNOT($a \rightarrow q_2$)
2. CNOT($b \rightarrow q_2$)

Step 3: Borrow Calculation

- Borrow occurs if $b = 1$ and $a = 0$:

borrow = $b \text{ AND } (\text{NOT } a)$

- Steps in Quirk:
 1. Apply X gate on a (to create NOT a)

2. Apply CCX (Toffoli) gate:
 - Controls: NOT a (q0) and b (q1)
 - Target: q2 or another qubit for borrow

This flips the target qubit only when borrow is needed.

Step 4: Measurement

- Measure:
 - Difference qubit \rightarrow classical bit c0
 - Borrow qubit \rightarrow classical bit c1